

Q1. Write VHDL code for the following:

1) D-flip-flop


D Flip Flop Entity

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity D_FLIP_FLOP is
5  port(
6      q: out std_logic;
7      clk: in std_logic;
8      synchronous_reset: in std_logic;
9      d: in std_logic
10  );
11
12 end D_FLIP_FLOP;
13
14 architecture behavioral of D_FLIP_FLOP is
15 begin
16
17     clocked_process: process(clk)
18     begin
19         if (rising_edge(clk)) then
20             if (synchronous_reset = '1') then
21                 q <= '0';
22             else
23                 q <= d;
24             end if;
25         end if;
26     end process clocked_process;
27 end behavioral;
```

D Flip Flop Test Bench

```
C:\Users\musil\OneDrive - Ohio University\First Year\Winter\Design of Digital Circuits\Module 9\D_flip_flop_modelSim
File Edit Search View Encoding Language Settings Tools Macro Run Plugins Window ?
D_FLIP_FLOP.vhd D_flip_test_bench.vhd
1  -- Mark Musil
2  -- This file describes a D flip flop and runs a few tests on it.
3
4  library ieee;
5  use ieee.std_logic_1164.all;
6
7  entity D_flip_flop_test_bench is
8  end entity;
9
10 architecture behavior of D_flip_flop_test_bench is
11
12     signal ext_d : std_logic := '1';
13     signal ext_q : std_logic;
14     signal ext_reset, ext_clk: std_logic := '0';
15
16     component D_FLIP_FLOP port(
17         clk, d, synchronous_reset : in std_logic;
18         q : out std_logic
19     ); end component;
20
21     begin
22
23     -- ext_clk <= NOT(ext_clk) after 5 ns;
24     -- ext_d <= NOT(ext_d) after 30 ns;
25     -- ext_reset <= NOT(ext_reset) after 50 ns;
26
27     DUT: D_FLIP_FLOP port map(
28         clk => ext_clk,
29         d => ext_d,
30         synchronous_reset => ext_reset,
31         q => ext_q);
32
33     clock_process: process
34     begin
35         ext_clk <= '0';
36         wait for 5 ns;
37         ext_clk <= '1';
38         wait for 5 ns;
39     end process;
40
41     stimulus: process
42     begin
43         wait for 10 ns;
44         ext_d <= '1';
45         wait for 10 ns;
46         ext_d <= '0';
47         wait for 10 ns;
48         ext_d <= '1';
49         wait for 10 ns;
50         ext_d <= '0';
51         wait for 10 ns;
52         ext_d <= '0';
53         wait for 10 ns;
54         ext_d <= '1';
55         wait for 10 ns;
56         ext_d <= '0';
57     end process;
58
59     reset_process: process
60     begin
61         wait for 30 ns;
62         ext_reset <= '1';
63         wait for 10 ns;
64         ext_reset <= '0';
65     end process;
66 end architecture behavior;
67
68
```

Simulation

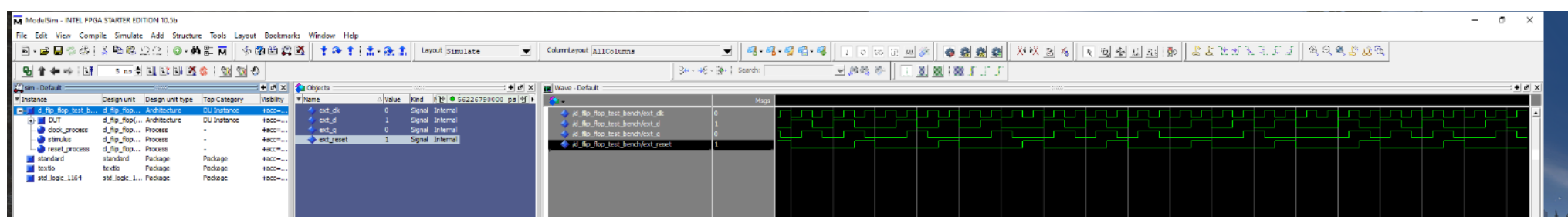

2) T-flip-flop


T Flip Flop Entity

```
C:\blog\Tutorials\modelSim\t_flip_flop\t_flip_flop.vhd - Notepad++
File Edit Search View Encoding Language Settings Tools Macro Run Plugins Window ?
t_flip_flop.vhd t_flip_flop_test_bench.vhd
1
2 library ieee;
3 use ieee.std_logic_1164.all;
4
5 entity t_flip_flop is port (
6     clk, t, asynch_reset : in std_logic;
7     q : out std_logic
8 );
9 end t_flip_flop;
10
11 architecture letsBehave of t_flip_flop is
12
13 begin
14
15     t_flip_flop_process: process(clk, asynch_reset) begin
16         if(asynch_reset = '1') then
17             q <= '0';
18         elsif rising_edge(clk) then
19             if(t = '1') then
20                 q <= NOT(q);
21             end if;
22         end if;
23     end process t_flip_flop_process;
24 end letsBehave;
```

T Flip Flop Testbench

```
t_flip_flop.vhd x t_flip_flop_test_bench.vhd x
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity t_flip_flop_test_bench is
5  end entity;
6
7  architecture pleaseBehave of t_flip_flop_test_bench is
8
9  signal external_t : std_logic := '1';
10 signal external_q : std_logic;
11 signal external_reset, external_clock: std_logic := '0';
12
13 component t_flip_flop port (
14     clk, t, asynch_reset : in std_logic;
15     q : out std_logic
16 ); end component;
17 begin
18
19     DUT: t_flip_flop port map(
20         clk => external_clock,
21         t => external_t,
22         asynch_reset => external_reset,
23         q => external_q);
24
25     clock_process: process
26     begin
27         external_clock <= '0';
28         wait for 5 ns;
29         external_clock <= '1';
30         wait for 5 ns;
31     end process;
32
33     test_stimuli: process
34     begin
35         wait for 10 ns;
36         external_t <= '0';
37         wait for 10 ns;
38         external_t <= '1';
39     end process;
40
41     reset_process: process
42     begin
43         wait for 60 ns;
44         external_reset <= '1';
45         wait for 30 ns;
46         external_reset <= '0';
47     end process;
48 end architecture pleaseBehave;
```

T Flip Flop simulation

 

3) 8-bit wide serial shift register with D-flip-flops

D Flip-Flop

Ln#	
1	
2	library ieee;
3	use ieee.std_logic_1164.all;
4	
5	entity D_FLIP_FLOP is
6	port(
7	q: out std_logic;
8	clk: in std_logic;
9	synchronous_reset: in std_logic;
10	d: in std_logic
11);
12	
13	end D_FLIP_FLOP;
14	
15	architecture behavioral of D_FLIP_FLOP is
16	
17	begin
18	
19	clocked_process: process(clk)
20	begin
21	if (rising_edge(clk)) then
22	if (synchronous_reset = '1') then
23	q <= '0';
24	else
25	q <= d;
26	end if;
27	end if;
28	end process clocked_process;
29	end behavioral;
30	


Eight-bit shift register

```
TB_eight_bit_shift_register.vhd x t_flip_flop.vhd x t_flip_flop.vhd x D_eight_bit_SR.vhd x
2  library ieee;
3  use ieee.std_logic_1164.all;
4
5  entity D_eight_bit_SR is port(
6      clock: in std_logic;
7      serial_in: in std_logic;
8      serial_out: out std_logic
9  );
10 end D_eight_bit_SR;
11
12 architecture behavioral of D_eight_bit_SR is
13
14     signal internal_bus : std_logic_vector(6 downto 0);
15
16     component D_FLIP_FLOP port(
17         clk: in std_logic;
18         d: in std_logic;
19         q: out std_logic
20     ); end component;
21
22 begin
23
24     D_FLIP_FLOP1: D_FLIP_FLOP
25     port map(
26         clk => clock,
27         d => serial_in,
28         q => internal_bus(0)
29     );
30
31     D_FLIP_FLOP2: D_FLIP_FLOP
32     port map(
33         clk => clock,
34         d => internal_bus(0),
35         q => internal_bus(1)
36     );
37
38     D_FLIP_FLOP3: D_FLIP_FLOP
39     port map (
40         clk => clock,
41         d => internal_bus(1),
42         q => internal_bus(2)
43     );
44
45     D_FLIP_FLOP4: D_FLIP_FLOP
46     port map(
47         clk => clock,
48         d => internal_bus(2),
49         q => internal_bus(3)
50     );
51
52     D_FLIP_FLOP5: D_FLIP_FLOP
53     port map(
54         clk => clock,
55         d => internal_bus(3),
56         q => internal_bus(4)
57     );
58
59     D_FLIP_FLOP6: D_FLIP_FLOP
60     port map (
61         clk => clock,
62         d => internal_bus(4),
63         q => internal_bus(5)
64     );
65
66     D_FLIP_FLOP7: D_FLIP_FLOP
67     port map (
68         clk => clock,
69         d => internal_bus(5),
70         q => internal_bus(6)
71     );
72
73     D_FLIP_FLOP8: D_FLIP_FLOP
74     port map (
75         clk => clock,
76         d => internal_bus(6),
77         q => serial_out
78     );
79
80 end behavioral;
81
```

Test bench

```
C:/Users/musil/OneDrive - Ohio University/First Year/Winter/Design of Digital Circuits/Module 9/8_t
Ln#
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity TB_eight_bit_shift_register is
5  end entity;
6
7
8  architecture behavioral of TB_eight_bit_shift_register is
9
10     signal TB_clock: std_logic := '0';
11     signal TB_serial_in: std_logic := '0';
12     signal TB_serial_out: std_logic;
13
14
15     component D_eight_bit_SR port (
16         clk: in std_logic;
17         serial_in: in std_logic;
18         serial_out: out std_logic
19     );
20 end component;
21
22 begin
23
24     DUT: D_eight_bit_SR port map(
25         clk => TB_clock,
26         serial_in => TB_serial_in,
27         serial_out => TB_serial_out
28     );
29
30     |
31     clock_process: process
32
33     begin
34         TB_clock <= '0';
35         wait for 5 ns;
36         TB_clock <= '1';
37         wait for 5 ns;
38     end process;
39
40     test_stimuli: process
41     begin
42         TB_serial_in <= '1';
43         wait for 10 ns;
44         TB_serial_in <= '0';
45         wait for 10 ns;
46         TB_serial_in <= '1';
47         wait for 10 ns;
48         TB_serial_in <= '0';
49         wait for 10 ns;
50         TB_serial_in <= '1';
51         wait for 10 ns;
52         TB_serial_in <= '0';
53         wait for 10 ns;
54         TB_serial_in <= '1';
55         wait for 10 ns;
56         TB_serial_in <= '0';
57         wait for 10 ns;
58     end process;
59
60 end behavioral;
```


Simulation Results

 

Q2. Do question 4.13 (chapter 4).

4.13. Find the errors in the following code:

```
architecture has_errors of design
begin
  p1: process
  begin
    if clk'event and clk = '1' then
      q <= a or b and c;
    end if;
  end;
end;
```

This block of VHDL is missing the following

- Entity declaration
 - Associated port declarations
- Process should be ended explicitly
- Has_errors should be ended explicitly
- The code should be declared with the clock in its sensitivity list

Correct Version

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity my_entity is
5  port (
6      a: in std_logic;
7      b: in std_logic;
8      c: in std_logic;
9      clk: in std_logic;
10     q: out std_logic
11 ); end my_entity;
12
13 architecture has_errors of my_entity is
14
15 begin
16
17     p1: process(clk)
18     begin
19         if clk='1' then
20             q <= ((a or b) and c);
21         end if;
22     end process p1;
23
24 end has_errors;
```

Q3. Do question 4.15 (chapter 4).


4.15. Do all processes require sensitivity lists? Can you declare a clocked process without a sensitivity list?

No. Without a sensitivity list the compiler cannot determine when to run the process. I attempted to run the fixed code from the previous problem without using a sensitivity list and the simulator could not start the simulation. See the simulator window below.

Without sensitivity list

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity my_entity is
5  port (
6      a: in std_logic;
7      b: in std_logic;
8      c: in std_logic;
9      clk: in std_logic;
10     q: out std_logic
11 ); end my_entity;
12
13 architecture has_errors of my_entity is
14
15
16
17 begin
18
19     p1: process
20     begin
21         if (clk'event and clk='1') then
22             q <= ((a or b) and c);
23         end if;
24     end process p1;
25
26
27 end has_errors;
```

Simulation without sensitivity list

 

However, when I added a sensitivity list, as shown in the code snippet below, the simulator ran well (also shown)

With sensitivity list

```
TB_eight_bit_shift_register.vhd x D_eight_bit_SR.vhd x 4p13.vhd x
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity my_entity is
5  port (
6      a: in std_logic;
7      b: in std_logic;
8      c: in std_logic;
9      clk: in std_logic;
10     q: out std_logic
11 ); end my_entity;
12
13 architecture has_errors of my_entity is
14
15 begin
16
17     p1: process(clk)
18
19         begin
20             if clk='1' then
21                 q <= ((a or b) and c);
22             end if;
23         end process p1;
24
25 end has_errors;
```

Simulation with sensitivity list

