

Problems

- 3.1. Write the entity declaration for a 2-bit equality comparator.
- 3.2. Write the entity declaration for the following architecture, assuming that all signals in the architecture are ports:

```

architecture write_entity of exercise2 is
begin
    mapper: process (addr) begin
        shadow_ram_sel <= '0';
        sram_sel <= '0';
        if addr >= x"0100" and addr < x"4000" then
            shadow_ram_sel <= '1';
        elsif addr >= x"8000" and addr < x"C000" then
            sram_sel <= '1';
        end if;

        promsel <= '0';
        if mem_mapped = '0' and bootup then
            prom_sel <= '1';
        end if;
    end process mapper;

    mem_mapped <= shadow_ram_sel or sram_sel;
end write_entity;

```

- 3.3. Write an entity declaration for each of the TTL devices in Table 2-1.
- 3.4. Write an entity declaration for a 4-bit magnitude comparator. Name the output port `al tb` for "a less than b."
- 3.5. Write four architecture bodies for the entity declaration of Problem 3.4: one using an `if-then-else` statement, one using Boolean equations, one using a `when-else` statement, and one using component instantiation statements and components similar to the `xnor2` and `and4` components of Listing 3-5. (Hint: the `<` symbol is used as a relational operator for "less than.")
- 3.6. Compile and synthesize to a CY7C371 the entity/architecture pairs for each of the first three descriptions that you generated in Problem 3.5. Open the report files and compare equations.